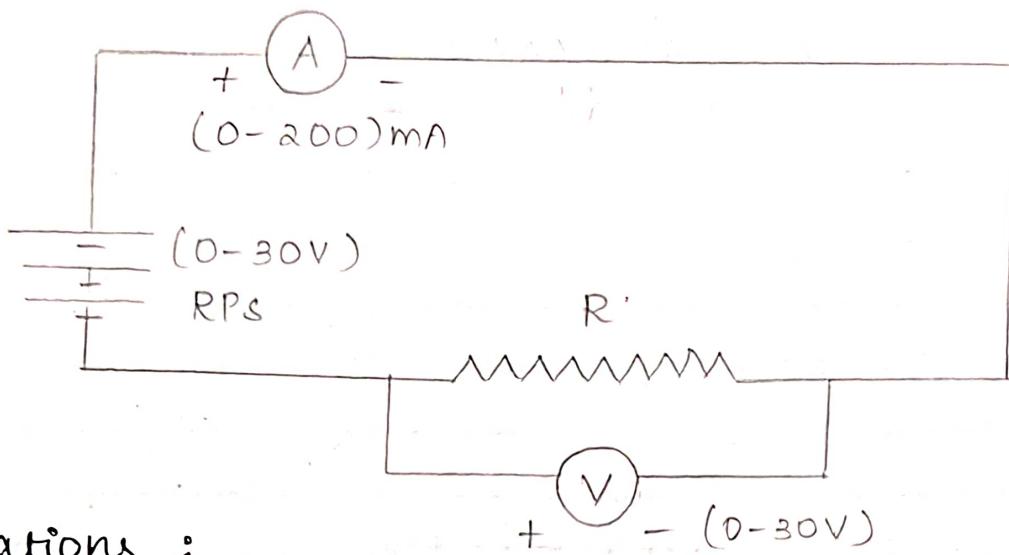


Circuit diagram :



Observations :

S. No	Voltage (V)	Current (mA)	$R = V/I$ in Ω
1.	2 V	3.4 mA	588.23 Ω
2.	3 V	5.4 mA	555.55 Ω
3.	4 V	7.4 mA	554.05 Ω
4.	5 V	9.3 mA	559.13 Ω
5.	6 V	10.1 mA	603.96 Ω

Model Calculation :


$$V = 2 \text{ V}$$

$$I = 3.4 \text{ mA}$$

$$R = V/R \Rightarrow \frac{2}{3.4 \times 10^{-3}}$$

$$R = 588.23 \Omega$$

Model graph :

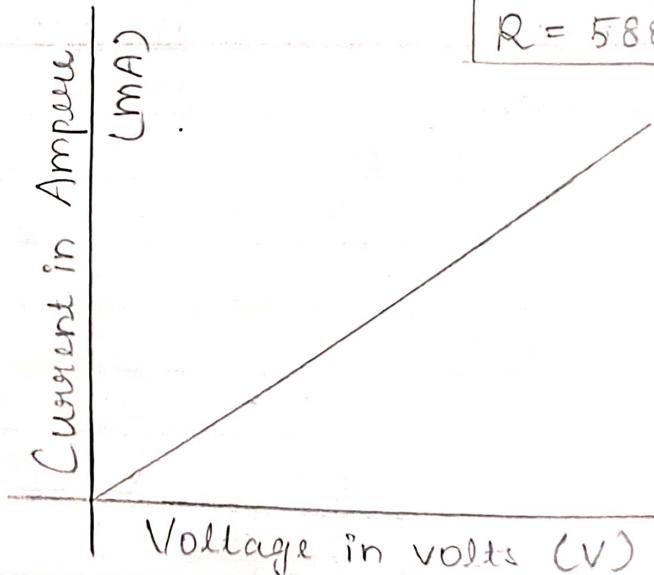

Ex. 01

Verification of Ohm's law & Kirchoff's Law

1.a) Verification of Ohm's law :

Aim:

To verify Ohm's law for a given resistive network.

Apparatus Required :

S.No.	Apparatus Name	Range	Quantity
1	RPS	(0-30)V	1
2	Ammeter	(0-200) mA	1
3	Voltmeter	(0-30) V	1
4	Resistors	INDIA 1 K Ω	1
5	Rheostat	300 Ω / 2A	1
6	Breadboard and Connecting wires	-	As per the Required


Procedure :

- ii) Make the connections as per circuit diagram
- iii) Switch ON the power supply to RPS and apply the voltage (10V) and take the reading of V and A.
- iii) Adjust the Rheostat in steps and take down the readings of ammeter and voltmeter.
- iv) Plot a graph with V along x-axis and I (y-axis)
- v) The graph will be a straight line verifies Ohm's law
- vi) Determine the slope of V-I graph.

Result :

Thus, the Ohm's law is verified for the given circuit.

Circuit diagram for KVL:

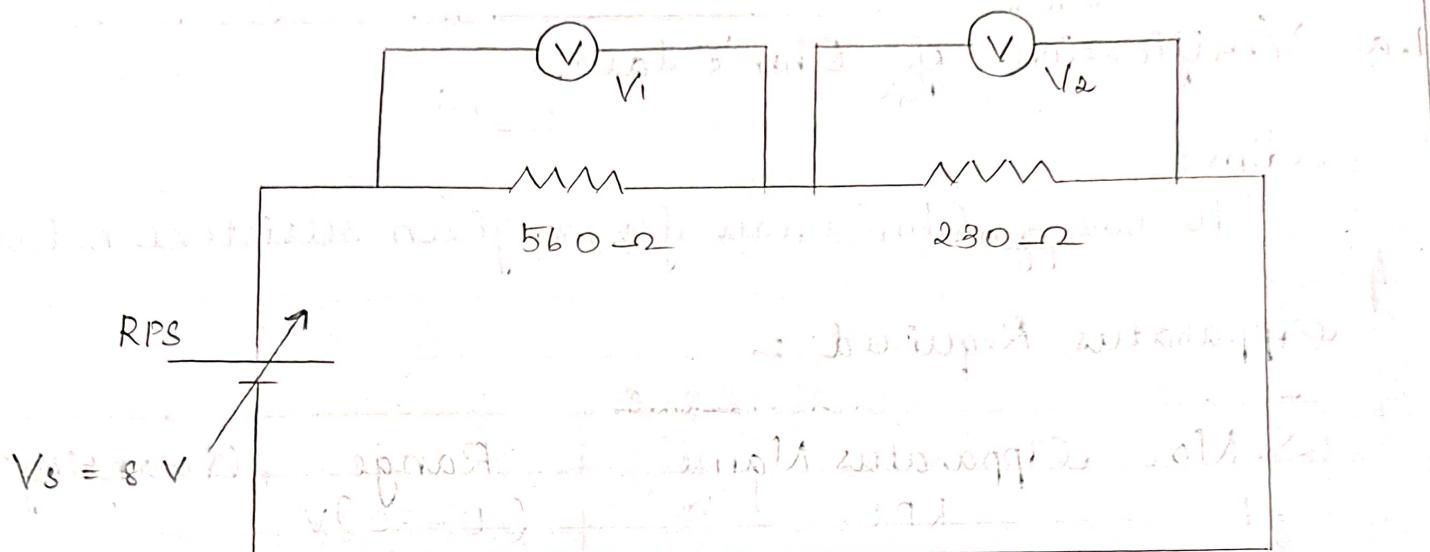

Tabulation for KVL:

Sl. No.	RPS voltage (V)	V_1 (volts)	V_2 (volts)	$V_1 + V_2 = V$
1.	8 V	5.67	2.32	7.99
2.	10 V	7.088	2.911	9.999

Supply voltage

$$V_s = V_1 + V_2 \rightarrow \textcircled{1}$$

By Voltage division rule,

$$V_{560\Omega} = \frac{8}{(560+230)} \times 560 = \frac{480}{790} = 5.67 \text{ V}$$

$$V_{230\Omega} = \frac{8}{(560+230)} \times 230 = \frac{180}{790} = 2.32 \text{ V}$$

Ex. 1.b) Verification of Kirchhoff's Law

Aim :

1. To verify Kirchoff's voltage law
2. To verify Kirchoff's Current law


Apparatus Required :

S. No.	Name of Equipment	Type	Range	QTY
1	RPS	-	-	1
2	Bread Board	-	-	1
3	Ammeters	MIC	0-10 & 0-5 MA	1
4	Voltmeters	MIC	0-10 & 0-15 MAV	1
5	Resistor	INDIA	170, 380, 4K0 & 1.7	1
6	Connecting wires	-	-	20

Procedure :

- (i) Connections are given as per the circuit diagram.
- (ii) Apply dc voltage to the circuit from the given RPS.
- (iii) Tabulate the voltmeters and ammeters using the reading from the experiment.
- (iv) Increase the voltage step by step to get different readings till the voltage reached upto 15 V.
- (v) Repeat step 3 for different values.
- (vi) Switch off the power supply after bringing RPS to the minimum voltage position.

Circuit diagram for KCL :

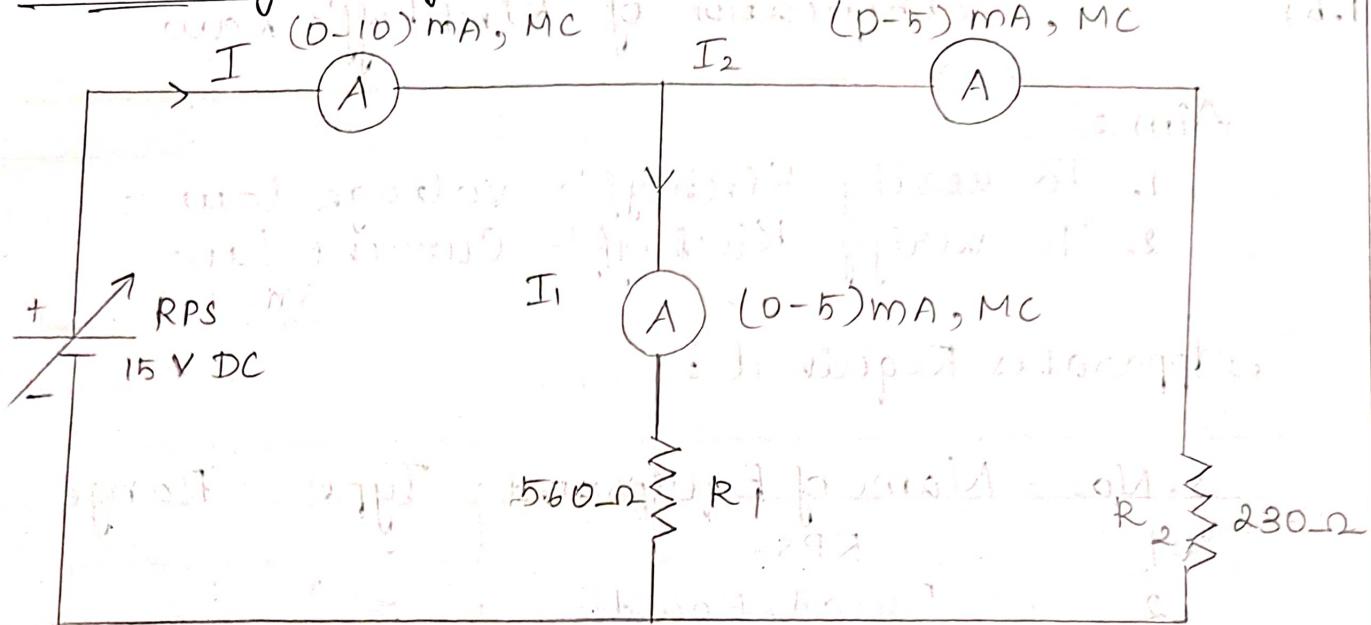

Tabulation for KCL :

S.No	RPS(V)	$\frac{I}{P}$	$\frac{I_1}{P}$	$\frac{I_2}{P}$	$\frac{I_1 + I_2}{P} = \frac{I}{P}$
1.	8 V	14.3	14.5	34.7	49
2.	10 V	17.8	17.1	43.4	61

Model Calculation :

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{560 \times 230}{560 + 230} = \frac{128800}{790} = 163.03\Omega$$

By current division rule,


$$I_1 = \frac{I_{total}}{R_{total}} \times R_{opp} = \frac{0.049}{(560 + 230)} \times 230 = 0.0142 \text{ A} = 14.2 \text{ mA}$$

$$I_{total} = \frac{V_s}{R_{eq}} = \frac{8}{163.03} = 0.049 \text{ A} = 49 \text{ mA}$$

$$I_2 = \frac{0.049}{560} \times 560 = 0.049 \text{ A} = 49 \text{ mA}$$

Precautions :

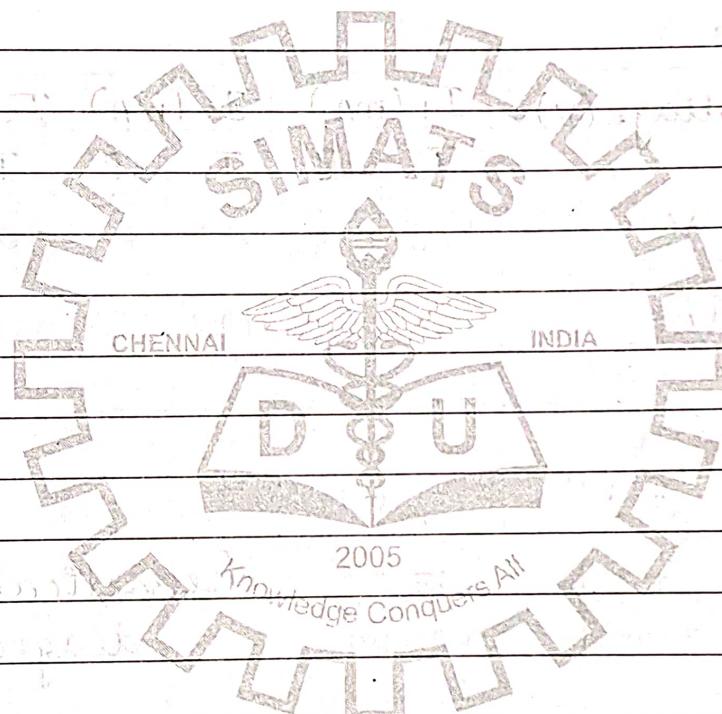
- (i) Keep RPS at maximum when switching ON and OFF the power supply.
- (ii) Connections should properly check before switch ON the supply.



Result :

Thus, the Kirchoff's voltage and current law is verified for the given circuit.

Circuit diagram :

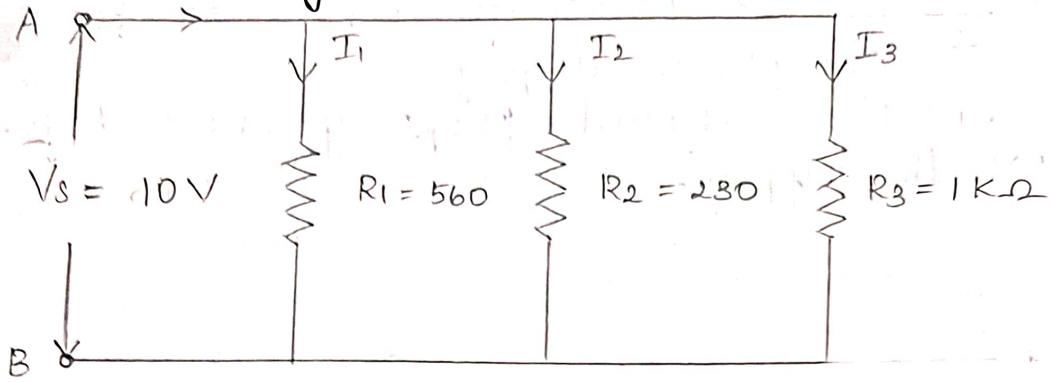


Tabulation :

S. No	RPS voltage (v)	I_1 (mA)		I_2 (mA)		I_3 (mA)		$I_{total} = I_1 + I_2 + I_3$	
		T	P	T	P	T	P	T	P
1.	10 V	17.8	14	43	41	10	7.5	70.8	62.5
2.	5 V	6.8	6.5	19.7	19.5	3.7	3.5	30.2	26

Calculation :

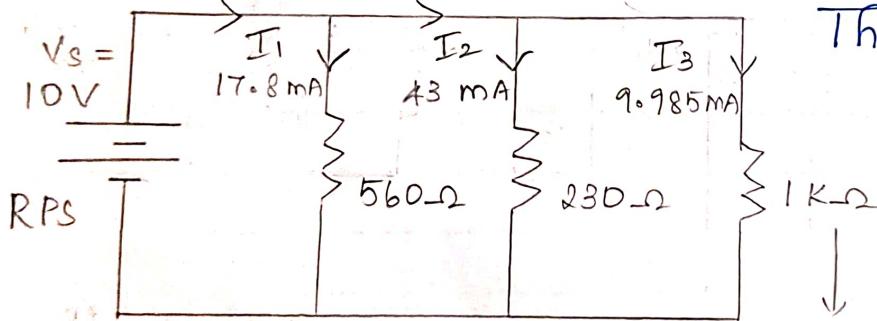
$$71.3 \text{ mA} \xrightarrow{\frac{I_1 + I_2 + I_3}{R_1 + R_2 + R_3}} 53.04 \text{ mA}$$



Theoretical
diagram

$$71.3 \text{ mA}$$

$$1\ K\Omega = 1000\ \Omega$$

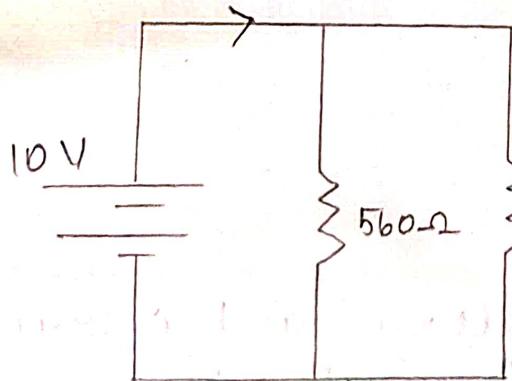

$$= \frac{230 \times 1000}{230 + 1000} = \frac{230000}{1230} = 186.99\ \Omega$$

Ex. 02

Calculation of individual branch current & total current drawn from the power supply

Aim :

To calculate the individual branch current and total current drawn from the power supply for the given parallel connected circuit.

Apparatus Required :


S.No	Name of the Item	Range	Quantity
1	Regulated power supply (RPS)	(0-30)V	1
2	Ruitors - 330Ω, 1KΩ, 5600Ω	-	Each 1
3	Bread Board	INDIA	3
4	Ammeter	-	1
5	Connecting wires	-	-
6			As required

Procedure :

- Connect the circuit as per the circuit diagram.
- Apply required value of DC supply voltage using the Regulated power supply (RPS).
- Note down the readings shown by all the ammeters.
- Repeat the procedure for different value of supply voltage if required.

Result :

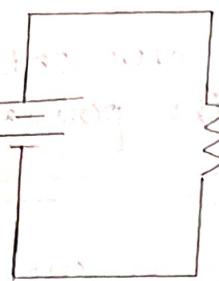Thus, the theoretical values of branch currents are verified practically.



$$\text{Req} = \frac{560 \times 186.99}{560 + 186.99} = \frac{104714.4}{746.99} = 140.18 \Omega$$

$$\text{Req} = 140.18 \Omega$$

$$I_{\text{total}} = \frac{V_s}{\text{Req}} = \frac{10}{140.18} = 0.0713 \text{ A} = 71.3 \text{ mA}$$

By Current division rule,

$$I_1 = \frac{I_T}{560 + 186.99} \times 186.99 = \frac{0.0713}{746.99} \times 186.99 = 0.0178 \text{ A} = 17.8 \text{ mA}$$


$$I_p = \frac{I_T}{560 + 186.99} \times 560 = \frac{0.0713}{746.99} \times 560 = 0.0534 \text{ A} = 53.4 \text{ mA}$$


By current division rule,

$$I_2 = \frac{I_p}{(280 + 1000)} \times 1000 = \frac{0.0534}{1280} \times 1000 = 0.043 \text{ A} = 43 \text{ mA}$$

$$I_3 = \frac{I_p}{(280 + 1000)} \times 280 = \frac{0.0534}{1280} \times 280 = 9.985 \times 10^{-3} \text{ A} = 9.985 \text{ mA}$$

Practical diagram:

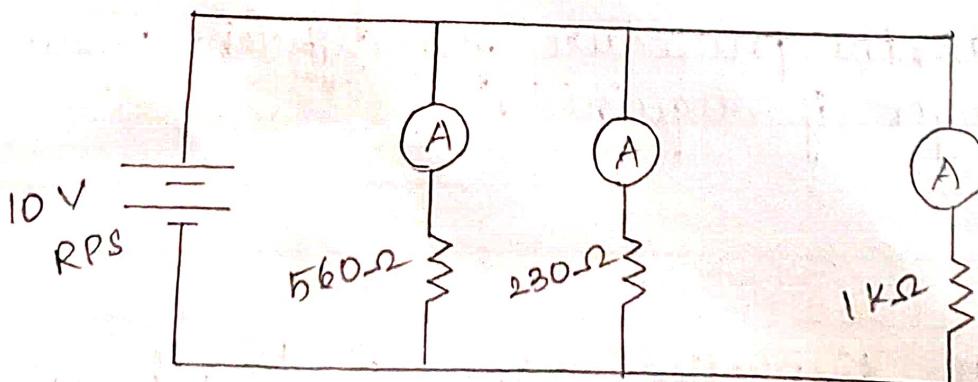

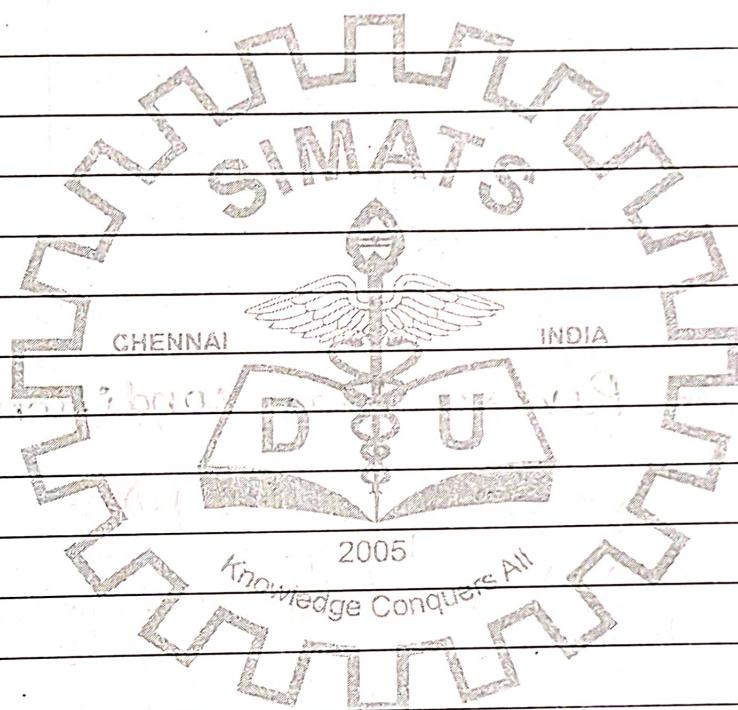

Result:

Thus, the theoretical value of Branch currents are verified practically.

Circuit diagram :

Figure 1 :- Forward Bias condition


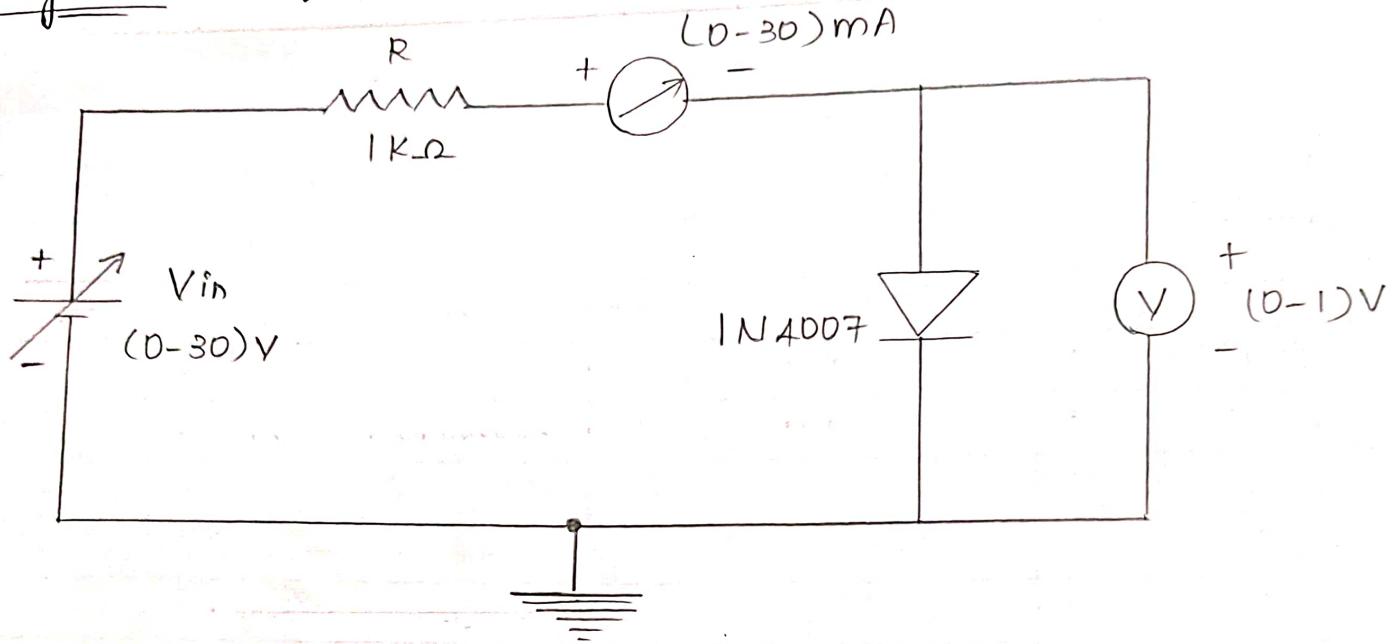


Figure 2 :- Reverse Bias condition

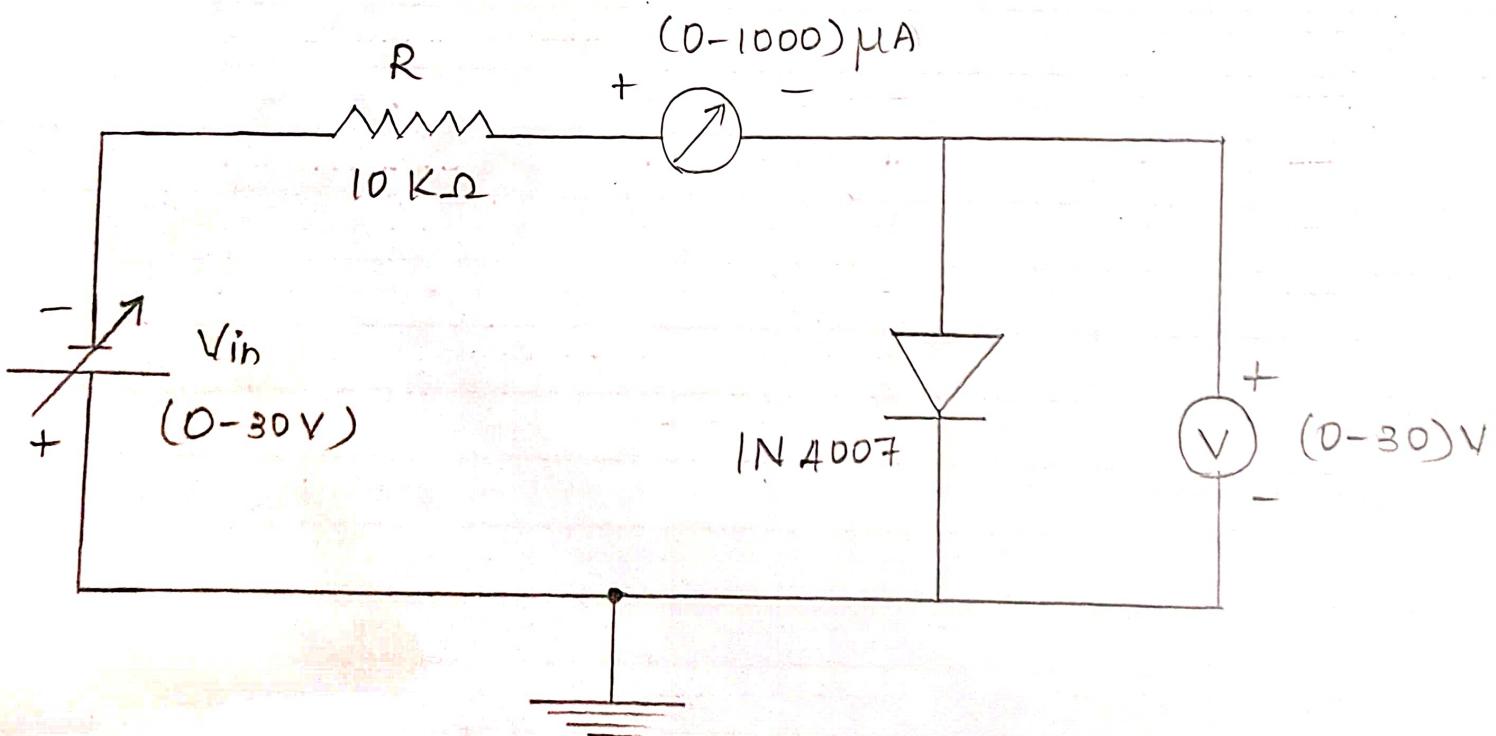

Ex.03

V-I Characteristics of PN Junction Diode

A)

Aim :

To plot the V-I characteristics of a PN junction diode in both forward and reverse directions.

Apparatus Required :

SL.No.	Apparatus	Range	Quantity
1	DC RPS	(0-30) V	1
2	Ammeter	(0-30) MA, (0-1000) μ A	1
3	Voltmeter	(0-1) V, (0-30) V	1
4	Diode	TN 4007	1
5	Resistors	1K Ω & 10K Ω	1 each
6	Bread board	-	1
7	Connecting wires	-	As required

Procedures:



Forward Biased Conditions :

- Connections are given as per the figure 1 using the silicon PN junction diode.
- Vary V_f gradually in steps of 0.1 volts and note down the corresponding reading of I_f .
- Step size is not fixed because of nonlinear curve and vary the x-axis variable.
- Tabulate the different forward currents obtained for different forward voltages.

Observations :


Forward Bias :

SL. NO.	RPS Voltage (V)	Forward - V_f (volts)	I_f (mA)
1.	0.2	0.2	0 mA
2.	0.4	0.4	0.5 mA
3.	0.5	0.5	1 mA
4.	0.56	0.56	1.4 mA
5.	0.6	0.6	7 mA
6.	0.64	0.64	16 mA
7.	0.66	0.66	20 mA
8.	0.66	0.66	26 mA

Reverse Bias :

SL. NO.	RPS Voltage (V)	Reverse - V_R (volts)	I_R (μA)
1.	0.5	0.5	10 μA
2.	10 μA to mA	1	25 mA
3.	$= 10 \times 10^{-3}$	1.55	45 mA
4.	$= 0.010$	2	65 mA
5.	$I_R = \text{Reverse current}$	3	95 mA
6.		4	130 mA
7.		6	190 mA


Model Waveform :

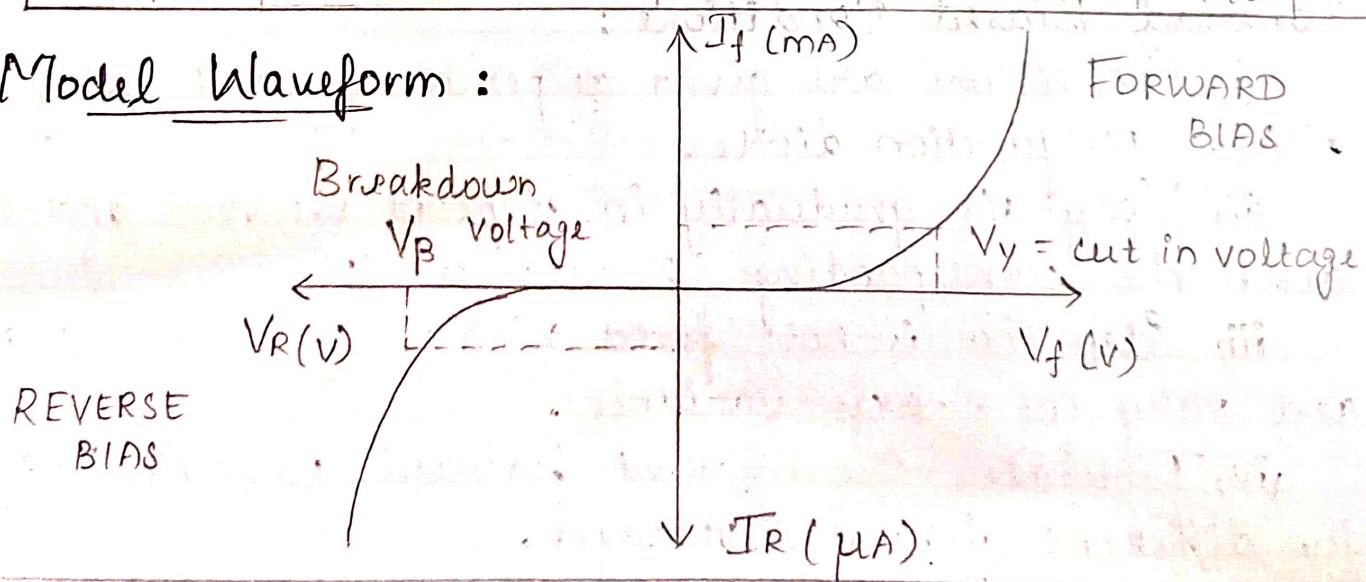



Reverse Biased conditions :

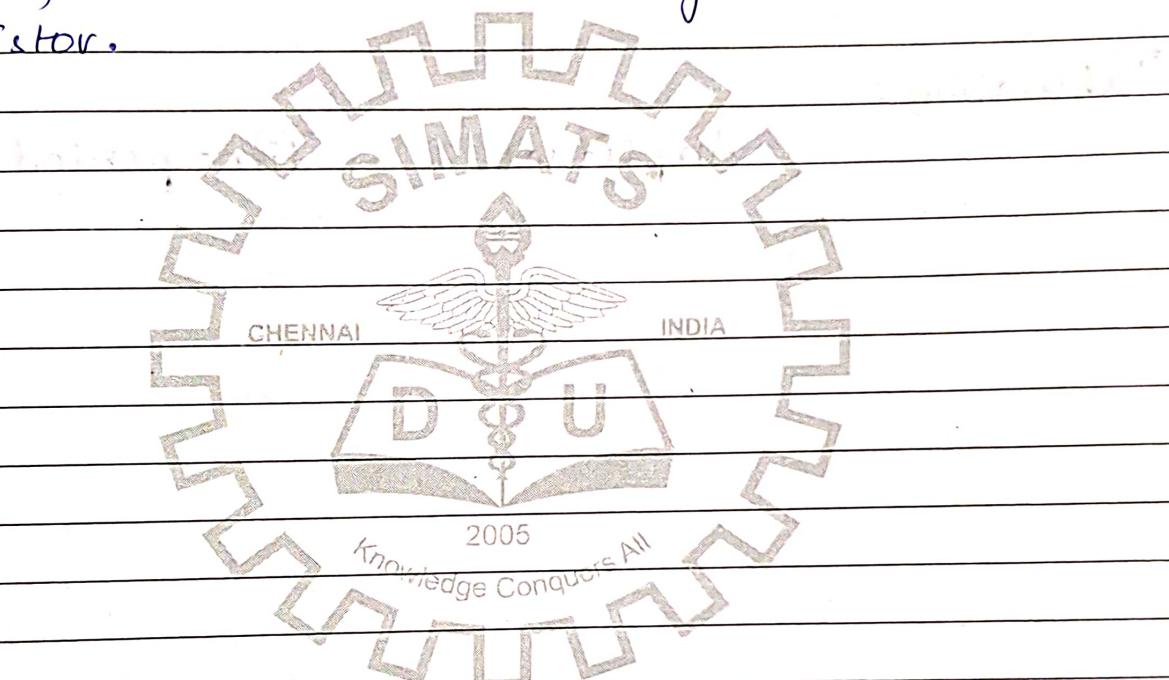
- (i) Connect the circuit as shown in figure 2 using silicon P-N junction diode.
- (ii) Vary V_R gradually in steps of 0.5 volts upto 8 volts and note down the corresponding readings of I_R .
- (iii) Tabulate the different reverse currents obtained for the different reverse voltages. ($I_R = V_R/R$, where V_R is the voltage across $10\text{ k}\Omega$ resistor.)



Result :

Thus, the Forward and Reverse bias V-I Characteristics of P-N diode was drawn and Observed.

Circuit diagram :

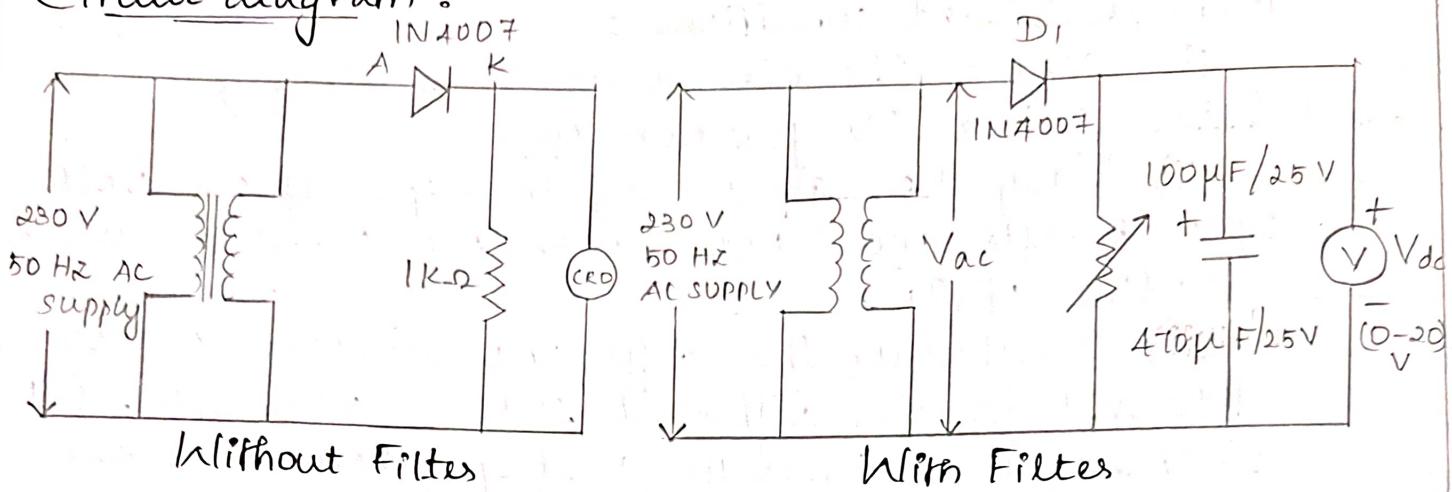


Tabulation :


Amplitude	Time period
1.5	0.5

Output graph :

Without Filters :

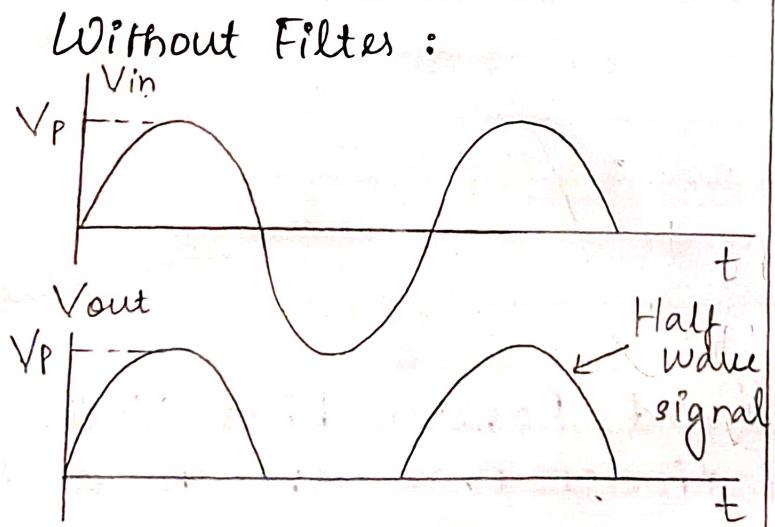

With Filter

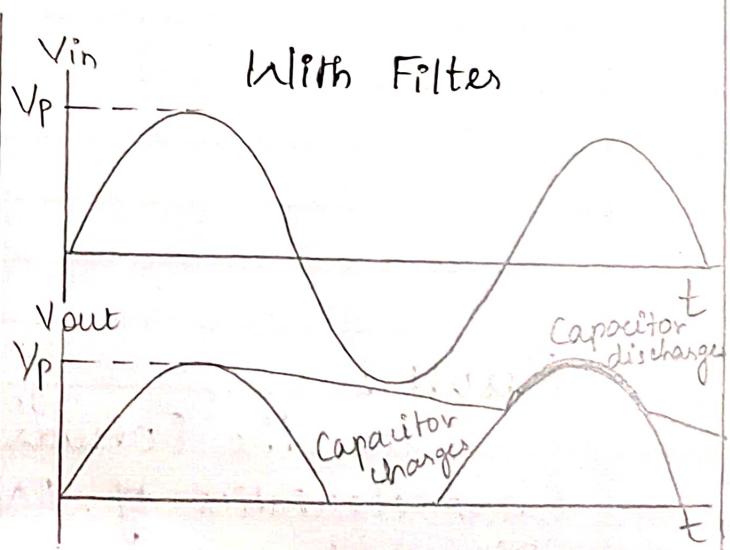

Ex. 03

Half Wave Rectifier

b) Aim :

To examine the input and output waveforms of half wave rectifiers with and without filter.

Apparatus Required :

Sl. No.	Apparatus	Range	Quantity
1	Diode	IN 4007	1
2	Transformers	6-0-6	1
3	Resistors	140-2	1
4	Connecting wires	-	As required
5	Breadboard	—	1
6	Capacitor	100 μF	1


Procedure :

- Connections are made as per the circuit.
- Connect the primary side of the transformer to ac mains and the secondary side to the rectifier input.
- By the multimeter, measure the ac input voltage of the rectifier and ac, and dc voltage at the output of the rectifier.
- Find the theoretical of dc voltage by using the formula $V_{dc} = V_m/\pi$.


Result :

Thus, the rectified output using half-rectifier is observed and verified.


Forward Bias

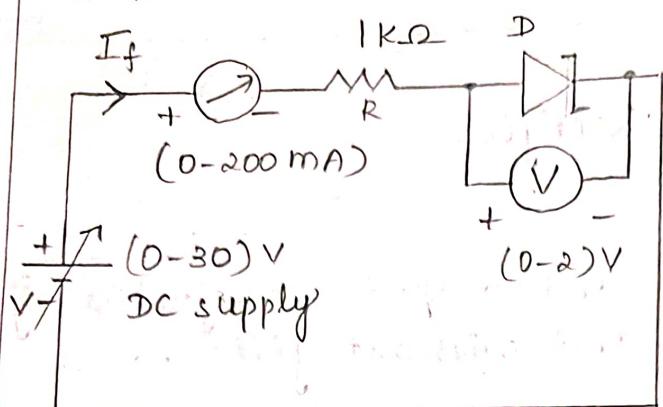


Reverse Bias

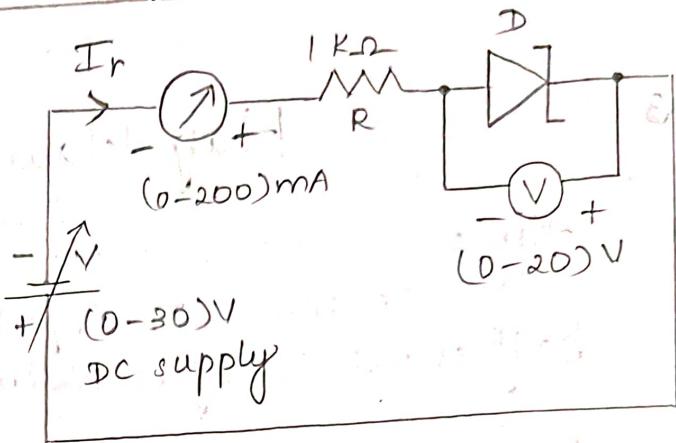

Voltage Regulation:


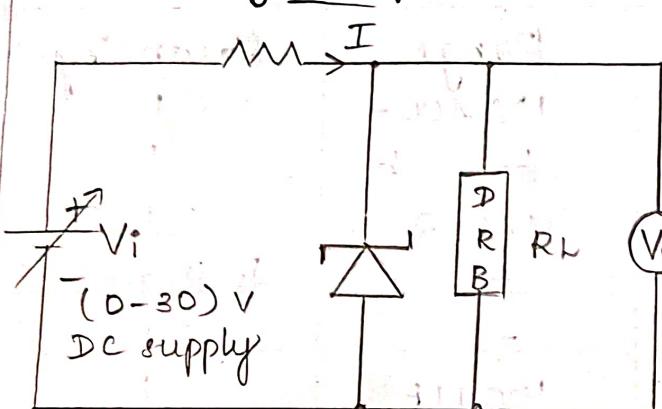


Model graph:

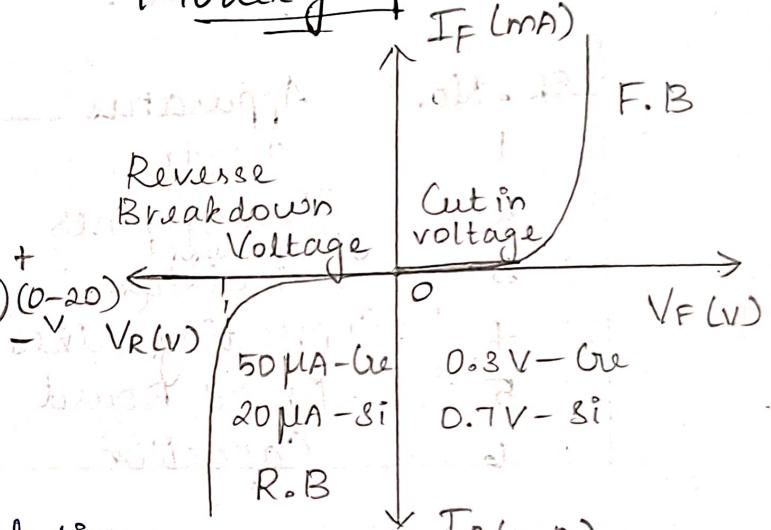

Zener diode Voltage Regulation

Load regulation Characteristics

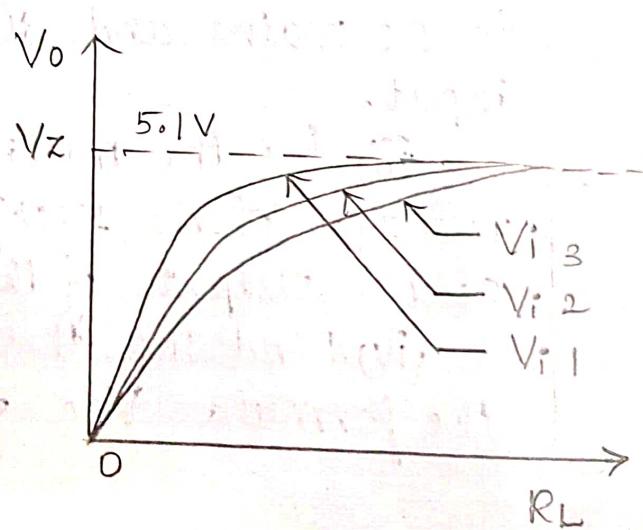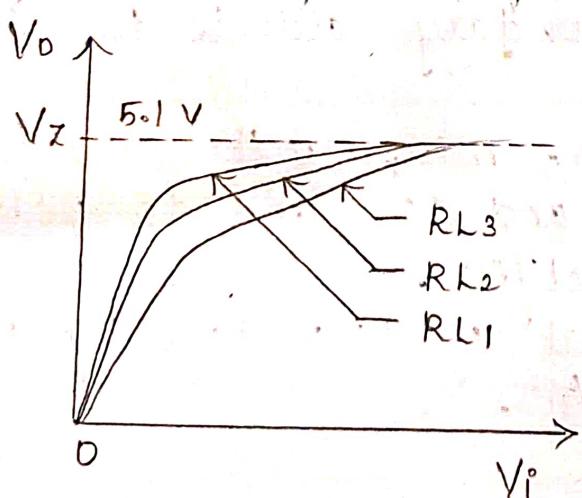

Voltage Regulation Characteristics Vi Versus Vo &
 RL Versus Vo .

Ex.04

V-I Characteristics Zener diode and Zener as Voltage Regulator

a) Aim :

- (i) To Obtain the forward bias and Reverse bias characteristic of a Zener diode.
- (ii) Find out the Zener Break down voltage from the characteristic.
- (iii) To obtain the Load Regulation Characteristic.

Apparatus required :

S.No.	Name of Apparatus	Range	Quantity
1	DC RPS	0-30 V	1
2	Diode	ECZ 5.1	1
3	Resistor	1 K Ω , 5600	Each 1
4	DC Ammeter	0-200 mA	1
5	DC Voltmeter	0-2V, 0-20V	Each 1
6	Decade Resistance Box	-	1
7	Bread board and wires	-	1 set

Procedure :

Forward Bias Characteristics :

1. Connect the circuit as per the circuit.
2. Switch on the RPS and slowly increase the source voltage.
3. Increase the diode current in steps of 2mA and note down the corresponding voltage across the Zener diode under forward Bias as per table given.

Tabulation :

Forward Bias

S.No.	V_F (Volts)	I_F (mA)
1	0.2 V	0 mA
2	0.4 V	0 mA
3	0.5 V	0.5 mA
4	0.6 V	0.5 mA
5	0.64 V	1 mA
6	0.68 V	2 mA
7	0.7 V	3 mA
8	0.7 V	10 mA
9	0.7 V	15 mA

Reverse Bias

S.No.	V_R (volts)	I_R (mA)
1	0.5 V	0 mA
2	1 V	0 mA
3	2 V	0 mA
4	3.5 V	0 mA
5	4.5 V	1 mA
6	4.5 V	1.5 mA
7	4.5 V	2.5 mA
8	4.5 V	10 mA
9	4.5 V	15 mA

Line and Load Regulations :

S.No.	R_L (Ω)	$V_{i1} = 5V$ $V_{i2} = 10V$ $V_{i3} = 15V$	$V_o(V)$	$V_i(V)$	$R_{L1} = 1k\Omega$ $R_{L2} = 2k\Omega$ $R_{L3} = 3k\Omega$	$V_o(V)$	$V_o(V)$
1	1 k Ω	5 V	5 V	5 V	5 V	5 V	5 V
2	2 k Ω	10 V	10 V	10 V	10 V	10 V	10 V
3	3 k Ω	15 V	15 V	15 V	15 V	15 V	15 V
4	4 k Ω	20 V	20 V	20 V	20 V	20 V	20 V
5	5 k Ω	25 V	25 V	25 V	25 V	25 V	25 V
6	6 k Ω	30 V	30 V	30 V	30 V	30 V	30 V
7	7 k Ω	35 V	35 V	35 V	35 V	35 V	35 V
8	8 k Ω	40 V	40 V	40 V	40 V	40 V	40 V
9	9 k Ω	45 V	45 V	45 V	45 V	45 V	45 V
10	10 k Ω	50 V	50 V	50 V	50 V	50 V	50 V
11	11 k Ω	55 V	55 V	55 V	55 V	55 V	55 V
12	12 k Ω	60 V	60 V	60 V	60 V	60 V	60 V
13	13 k Ω	65 V	65 V	65 V	65 V	65 V	65 V
14	14 k Ω	70 V	70 V	70 V	70 V	70 V	70 V
15	15 k Ω	75 V	75 V	75 V	75 V	75 V	75 V
16	16 k Ω	80 V	80 V	80 V	80 V	80 V	80 V
17	17 k Ω	85 V	85 V	85 V	85 V	85 V	85 V
18	18 k Ω	90 V	90 V	90 V	90 V	90 V	90 V
19	19 k Ω	95 V	95 V	95 V	95 V	95 V	95 V
20	20 k Ω	100 V	100 V	100 V	100 V	100 V	100 V

4. Take the readings until a diode current of 20 mA.

5. Plot the graph V_F versus I_F .

Reverse Bias Characteristics :

- Connect the circuit as per the circuit diagram.
- Switch on the RPS and slowly increase V_s .
- Increase the diode current in steps of 2mA and note down the corresponding voltages.
- Take the readings until a diode current of 20mA.
- Plot the graph V_R versus I_R .

Load Regulation characteristics :

- Connect the circuit as per the circuit diagram
- By changing the R_L , kept constant I/P voltage at 5V, 10V, 15V as per given table.
- Now, By changing the I/P voltage, kept const. load Resistance at 1K, 2K, 3K as per table.

Zener Breakdown voltage :

Draw a tangent on the reverse bias of the Zener diode starting from the knee, and touching most of the points of the curve. [Zener Breakdown voltage]

Result :

Thus, the characteristics of Forward & Reverse bias and the Breakdown voltage are observed.

Zener Breakdown voltage =

Forward Bias Resistance =

Reverse Bias Resistance =